

Ollscoil na hÉireann, Gaillimh

National University of Ireland, Galway

SEMESTER II EXAMINATIONS, 1999/2000

THIRD YEAR ELECTRONIC ENGINEERING  
THIRD YEAR MECHANICAL ENGINEERING

ELECTRICAL POWER AND MACHINES

Professor L.E. Davis  
Professor D.J. Wilcox  
Professor W.G. Hurley

Duration of examination: *One Hour Thirty Minutes*

Instructions: Answer *three* questions

$$\mu_0 = 4\pi \times 10^{-7} \text{ H/m} \quad 1 \text{ hp} = 746 \text{ W}$$

- Q1. Derive an expression for the power in a three-phase balanced load in terms of line voltages and line currents.

The input power to a 3-phase induction motor is measured by the two-watt meter method. The readings were 6.7 kW and -1.8 kW and the line voltage was 400 V. Calculate:

- (a) the total active power
- (b) the power factor
- (c) the line current

- Q2. Explain why the third or triplen harmonics do not cancel in the neutral of a balanced three-phase system.

The load in Fig.1 is a rectifier with a capacitor filter. The load is balanced, the output current is 50A and the output ripple is 10% giving an input power factor of 0.42.

- (a) Calculate the line current  $I_a$
- (b) Calculate the neutral current  $I_n$

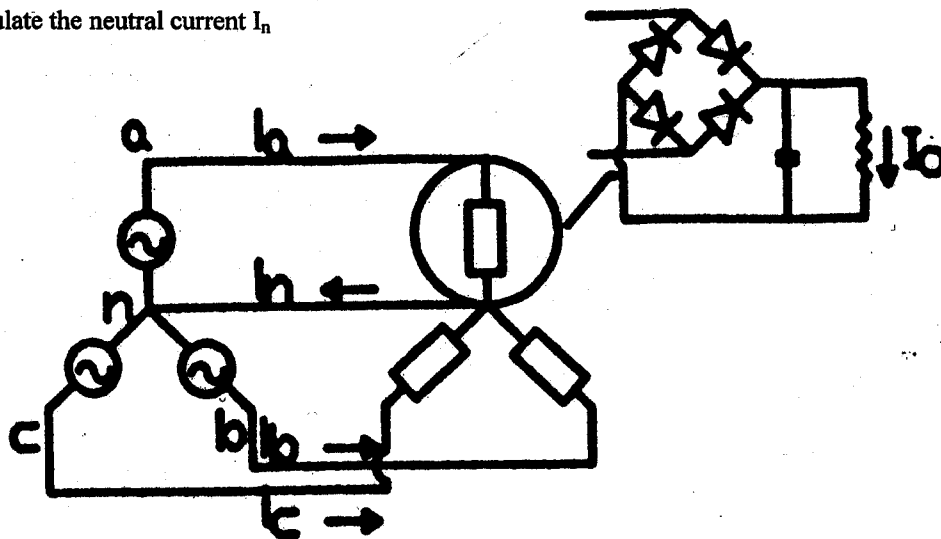


Fig. 1 Three-phase rectifier

Q3. Explain how a rotating flux wave is produced in a 3-phase induction motor.

A three-phase, 240v, 50Hz, six-pole induction motor has the following equivalent circuit parameters:

$$R_1 = 0.075 \, \Omega, \quad R_2 = 0.11 \, \Omega, \quad L_1 = L_2 = 0.25 \text{mH}, \quad L_m = 15 \text{mH}$$

- (a) Draw the equivalent circuit and show component values.
- (b) The motor drives a fan. The torque required for the fan varies as the square of the speed and is given by:

$$T_{\text{fan}} = 12.7 \times 10^{-3} \, \omega_m^2 \, \text{Nm}$$

Determine the speed of the fan when the motor is connected to a three-phase, 240 V, 50 Hz supply.

Q4. Describe one of the following motors under the headings:

- Principle of Operation
- Motor Characteristics
- Applications

- (a) Reluctance Motor
- (b) Universal Motor