

OLLSCOIL NA hÉIREANN
THE NATIONAL UNIVERSITY OF IRELAND, GALWAY

SEMESTER II (SPRING) EXAMINATIONS, 2000/2001

THIRD YEAR ELECTRONIC ENGINEERING
THIRD YEAR ELECTRONIC & COMPUTER ENGINEERING

SEMICONDUCTOR TECHNOLOGY (EE315)

Professor L.E. Davis
Professor D.J. Wilcox
Dr. F. Morgan

Duration of Examination : **2 hours**

Instructions: Answer **THREE** questions.
All questions carry equal marks.

$$I_{ds}(lin) = \mu \cdot C_{ox} \frac{W}{L} \left[(V_{gs} - V_{th}) V_{ds} - \frac{1}{2} V_{ds}^2 \right] \quad I_{ds}(sat) = \mu \cdot C_{ox} \frac{W}{2L} (V_{gs} - V_{th})^2$$

1. For the nMOS inverter of figure 1, calculate the following (clearly state and verify transistor operation modes in each case) :
- the inverter output 'low' voltage (6 marks)
 - the current through each transistor in steady state when (3 marks)
 - output is low
 - output is high
 - the input voltage to cause inverter output voltage (V_{out}) = 3.7V (4 marks)

 


Figure 1

- the inverter switching voltage (V_{inv}), assuming that both transistors operate in saturation at the inversion point. (3 marks)
- the current flowing at the inverter switching point. (2 marks)
- Illustrate (with a sketch) the effect of decreasing the Z_{pu}/Z_{pd} ratio on the inverter characteristic. (2 marks)

2. a) Briefly outline the typical nMOS fabrication process steps. Illustrate with a detailed sketch. (3 marks)
- b) Explain why an nMOS transistor is used as the pulldown device in a CMOS inverter while a pMOS transistor is used as the pullup device. (5 marks)
- c) Illustrate how CMOS technology offers improvements over nMOS-only technology (2 marks)
- d) Calculate the CMOS inverter switching voltage (V_{inv}) for the following CMOS inverter transistor parameters : $V_{thpd} = -V_{thpu} = 1V$, $W_{pd}/L_{pd} = 2$, $W_{pu}/L_{pu} = 4$, $\mu_n = 2\mu_p$, $V_{dd} = 5V$
Clearly state (and verify) transistor operation modes (4 marks)
- e) Illustrate the advantage that can be gained by implementing a CMOS logic circuit using NAND gates rather than NOR gates (3 marks)
- f) Highlight and comment on five aspects of MOS technology scaling. (3 marks)

3. a) Design a CMOS combinational logic circuit to implement the following function:

$$F = A.\overline{B} + C.D.(B + \overline{C}) \quad \text{Do not attempt any minimisation.} \quad (3 \text{ marks})$$

Indicate the required modifications to your CMOS logic circuit to convert it to an nMOS implementation (do not re-draw the circuit). (1 mark)

- b) Draw the equivalent coloured mask stick diagram for the CMOS mask layout of figure 3 (provided on separate page) [Input signals : A, B, C. Output signal F] (4 marks)
- c) Draw the MOS transistor level circuit diagram for the implementation of figure 3 and derive the boolean description for the circuit (5 marks)
- d) Sketch the device layer profile for the section through the line L---L in figure 3. Label all regions (e.g., silicon type, SiO₂ (gate & field), polysilicon gate, metal etc). (3 marks)
- e) Sketch and explain the basic operation and application of a conventional BiCMOS inverter circuit. List typical BiCMOS applications. (4 marks)
4. a) Describe the operation of a CMOS transmission gate and comment on how it is superior to nMOS and pMOS pass transistors. (4 marks)
- b) Illustrate an EXCLUSIVE-OR function implemented using transmission gates. Include a detailed truth table to illustrate the precise operation of the circuit. (4 marks)
Compare the number of transistors required to implement the EX-OR gate using
- transmission gates
 - CMOS gates
- (3 marks)
- c) Illustrate a full adder functions implemented using transmission gates. (5 marks)
- d) Describe latchup in BiCMOS circuits. Outline two methods used to minimise the occurrence of latchup (4 marks)