

OLLSCOIL NA hÉIREANN, GAILLIMH
NATIONAL UNIVERSITY OF IRELAND, GALWAY

SUMMER EXAMINATIONS, 2001

FIRST ELECTRONIC ENGINEERING
FIRST ELECTRONIC AND COMPUTER ENGINEERING
SECOND MECHANICAL ENGINEERING
SECOND BIOMEDICAL ENGINEERING

ANALOGUE ELECTRONICS

Professor L. E. Davis
Professor D. J. Wilcox
Mr. F. C. O'Malley

Duration of examination: *Two* hours

Instructions: Answer *four* questions

- Using Kirchoff's Laws determine the voltage V_{AB} in the circuit of figure 1 below. Specify also, the power dissipated in the resistor labelled R in the circuit.

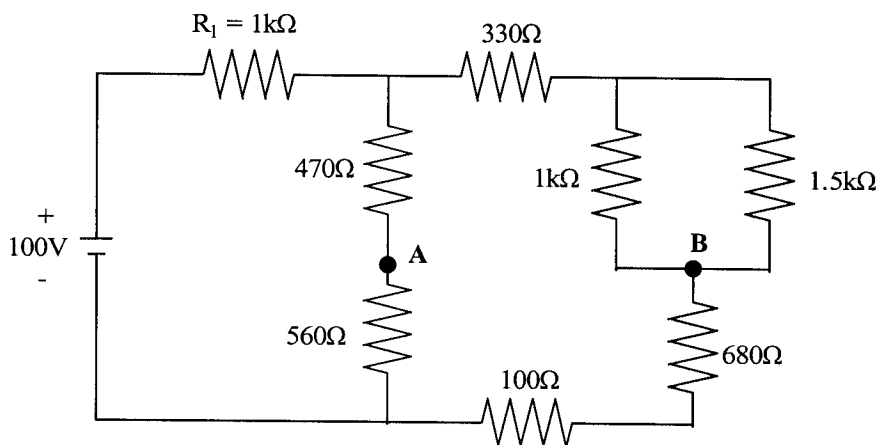


Figure 1

[25 marks]

2. Use the principle of superposition to determine the voltage across the $1.5\text{k}\Omega$ resistor in the circuit of figure 2.

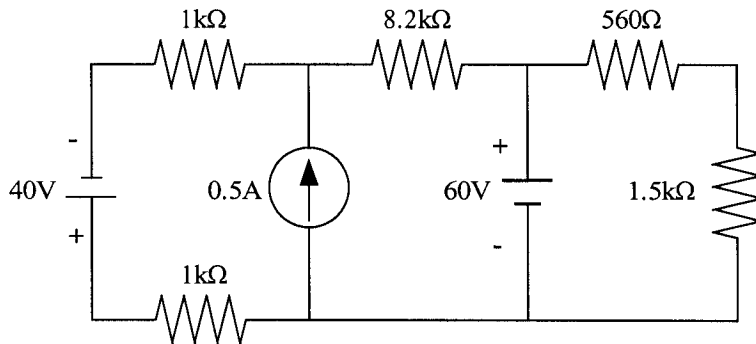


Figure 2

[25 marks]

3. (a) A voltmeter and an ammeter are two commonly used laboratory instruments. Describe the important electrical qualities each meter must possess for them to be useful as measuring instruments.

[5 marks]

- (b) (i) Determine the Thévenin equivalent of the circuit inside the dotted box of figure 3 (without the load resistor R_L attached).
(ii) Proceed to use the Thévenin equivalent to predict the voltage across R_L if it was attached to terminals A and B of the circuit.
(iii) What value of load resistor would allow maximum power to be delivered from the circuit.

[20 marks]

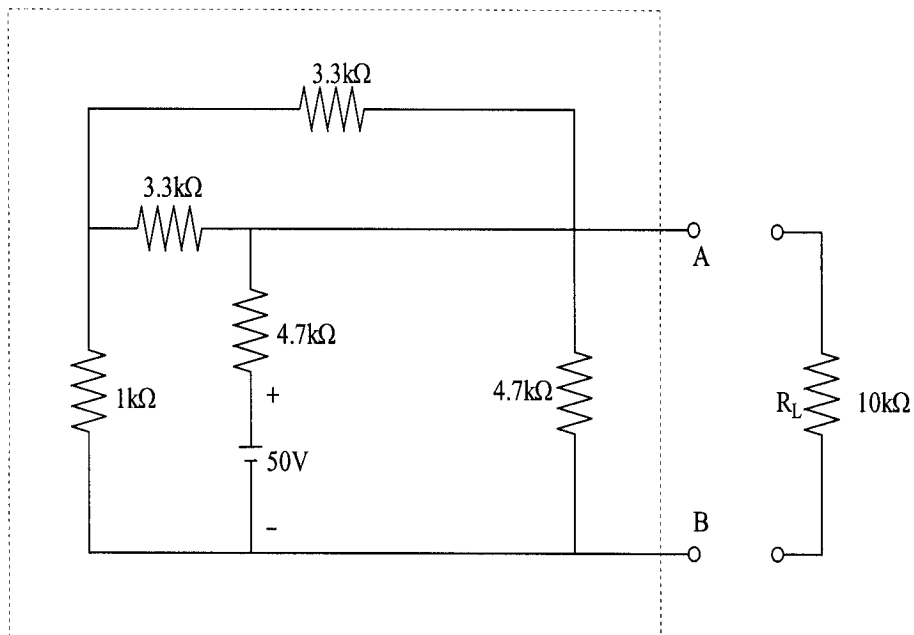


Figure 3

4. (a) The circuit of figure 4.1 shows a series connected RC circuit. Determine the magnitude and angle of the currents I_R and I_C and plot them on a phasor diagram. Calculate the magnitude and phase angle of the supply current I_s , and plot also on the phasor diagram.

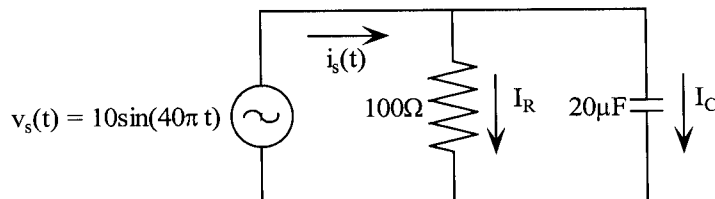


Figure 4.1

[12 marks]

- (b) The magnitude and phase of the current in the circuit of figure 4.2 is to be equivalent to the supply current I_s , of figure 4.1. Calculate the value of R and C of this circuit.

[13 marks]

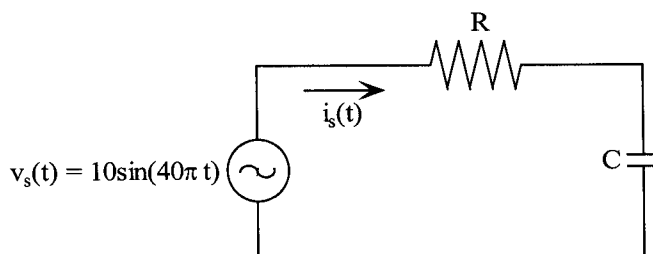


Figure 4.2

5. (a) Explain what is meant by the term *resonance* when referring to electrical circuits. Describe the conditions that exist when a series RLC circuit is in a state of resonance.

[5 marks]

- (b) A certain series resonant circuit has a maximum current of 50mA and an inductor voltage $V_L=100V$. If the supply voltage is 10V, calculate the magnitude of the total impedance Z and specify the magnitude values of X_C and X_L .

[7 marks]

- (c) Using Phasor analysis determine the magnitude of the supply current I_s of the circuit of figure 5 below. Specify the phase angle between the supply voltage and current.

[8 marks]

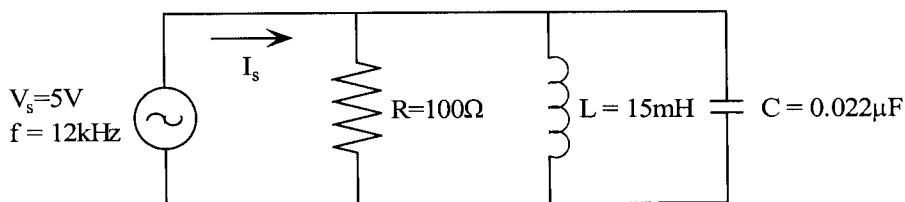


Figure 5

6. (a) Derive an expression for the rms value of a full-wave rectified sinusoidal signal of period T and peak voltage V_p .

[7 marks]

- (b) The circuit of figure 6 shows a half wave rectifier. Plot two cycles of the output voltage $v_o(t)$ and output current $i_o(t)$. What is the power dissipated in the $1\text{k}\Omega$ load resistor.

[6 marks]

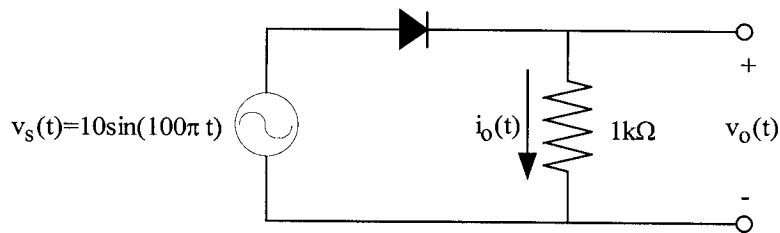


Figure 6

- (c) A smoothing capacitor is to be added to the circuit. Calculate the value of capacitance necessary in order to keep the ripple of the output voltage below 1%.

Plot two cycles of the smoothed output voltage waveform. Specify an approximation to the average output voltage when the smoothing capacitor is attached.

[7 marks]