

Semester II Examinations, 2002/2003
Front Page Template

Exam Code(s) 3BN121, 3BM121

Exam(s) Third Year Electronic Engineering
Third Year Mechanical Engineering

Module Code(s) EE302

Module(s) Electrical Power and Machines

Paper No. 2
Repeat Paper Special Paper

External Examiner(s) Professor S. McLaughlin
Internal Examiner(s) Professor D.J. Wilcox
Dr. M. Duffy

Instructions: Answer three questions
 $\mu_0 = 4 \pi \times 10^{-7} \text{ H/m}$

Duration 2hrs
No. of Answer books 1

Requirements:

Handout _____
MCQ _____
Statistical Tables _____
Graph Paper _____
Log Graph Paper _____
Other Material _____

No. of Pages 3
Department(s) Electronic Engineering

1. Draw a phasor diagram to illustrate the relationship between phase voltages and line currents for a balanced 3-phase, delta-connected load with lagging power factor. [6 marks]

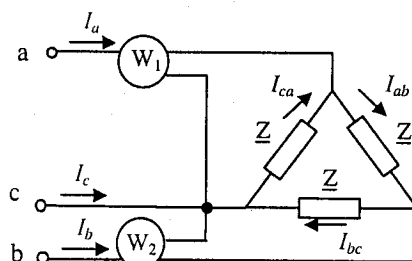


Fig. 1. Balanced 3-phase, delta-connected load

The balanced 3-phase delta-connected load shown in Fig. 1 has an impedance per phase of $Z = (15.5 + j7.5) \Omega$. The load is connected to a balanced 3-phase, 415 V supply. Taking $\underline{V}_{ab} = 415 \angle 30^\circ$:

- (a) Calculate the phase currents. [6 marks]
 - (b) Calculate the line currents. [6 marks]
 - (c) What is the total power delivered to the load ? [6 marks]
 - (d) Determine the wattmeter readings, W_1 and W_2 . [9 marks]
2. The magnetizing impedance of a 440 V, 50 Hz, 960 rpm, 3-phase induction motor is given as $R_m = 200 \Omega$, $X_m = 980 \Omega$. Locked rotor tests on the motor gave the following results :

$$V = 243.5 \text{ V}, \quad I = 20.2 \text{ A}, \quad T = 4.68 \text{ Nm}, \quad P = 1102 \text{ W}$$
 - (a) Draw the approximate equivalent circuit model of the motor referred to the stator side. [15 marks]
 - (b) Calculate the full load current drawn from the supply. Include the contribution of magnetising current in this case. [10 marks]
 - (c) Given that mechanical losses of 1500 W were deduced from no-load tests, determine the torque provided to a mechanical load running at rated speed. [8 marks]
 3. Answer *each* of the following questions :
 - (a) Describe the construction and basic operation of a permanent magnet stepper motor. [11 marks]
 - (b) Derive an equation to describe the speed-torque characteristic of a universal motor operated under AC conditions. [11 marks]
 - (c) Describe how a switched reluctance motor can be modeled as a variable inductor. [11 marks]

4. What is meant by voltage distortion in a power system ? Describe how such distortion is caused. [5 marks]

The load shown in Fig. 4 is provided with a distorted voltage waveform, $e(t)$, from a 50 Hz supply, where :

$$e(t) = 200\sin(\omega t) + 50\sin(3\omega t + 25^\circ)$$

- (a) Write the corresponding equation for the current waveform drawn by the load. [10 marks]
- (b) Calculate (i) the rms source voltage, (ii) the rms source current. [5 marks]
- (c) Calculate the average power delivered to the load. [8 marks]
- (d) What is the power factor of the source ? [5 marks]

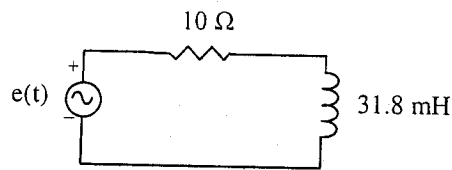


Fig. 4 : Linear RL load