

**OLLSCOIL NA hÉIREANN**  
**THE NATIONAL UNIVERSITY OF IRELAND, GALWAY**

**SUMMER EXAMINATIONS 1999**

**THIRD YEAR ELECTRONIC ENGINEERING EXAMINATION**

**ELECTRONIC DEVICES AND CIRCUITS**

Professor L.E. Davis  
 Professor D.J. Wilcox  
 Dr. F. Morgan

Duration of Examination : 3 hours

**Instructions**

Answer **FIVE** questions.  
 All questions carry equal marks.

1. An asymmetrical junction silicon diode has an extrinsic concentration of  $10^{17} \text{ cm}^{-3}$  on the N side and  $10^{16} \text{ cm}^{-3}$  on the P side. Under thermal equilibrium conditions at  $27^\circ\text{C}$ , calculate

- a) the built-in potential across the space charge layer (6 marks)
- b) the maximum electric field intensity inside the space charge layer (6 marks)
- c) the distances the space charge layer extends into the P and N regions. (8 marks)

Boltzmann's constant,  $k = 8.614 \times 10^{-5} \text{ eV}^\circ\text{K}$

Intrinsic carrier concentration (at  $27^\circ\text{C}$ ) =  $1.4 \times 10^{10} \text{ cm}^{-3}$

$\epsilon = 11.8 \epsilon_0$

$\epsilon_0 = 8.854 \times 10^{-14} \text{ F/cm}$

$q = 1.6 \times 10^{-19} \text{ C}$

2. a) The resistivity of pure germanium at a particular temperature is  $52 \text{ ohm-cm}$ . If it is doped with  $10^{14} \text{ atoms/cm}^3$  of a trivalent impurity, estimate the new value of resistivity. Assume mobilities  $\mu_n = 3800 \text{ cm}^2/\text{Vsec}$ ,  $\mu_p = 1800 \text{ cm}^2/\text{Vsec}$  and electronic charge  $q = 1.6 \times 10^{-19} \text{ C}$  (9 marks)
- b) Compare the DC behaviour of the following BJT-based transistor circuits (fig 2). Sketch the  $I_{ds}/V_{ds}$  characteristic and Q point of each device and indicate the mode of operation of each device. (11 marks)

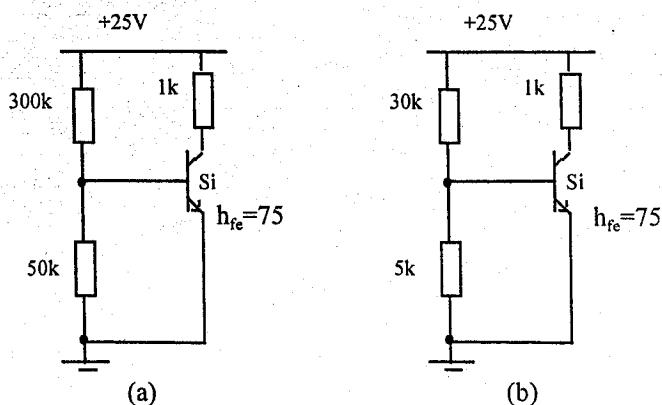


Figure 2 Common Emitter Amplifier DC bias circuits

3. The circuit of figure 3 shows a typical common emitter amplifier.

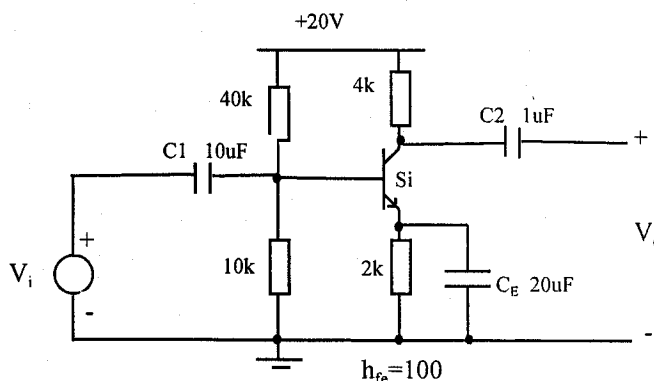


Figure 3 Common Emitter Amplifier

- Calculate the d.c. operating point of the amplifier (6 marks)
- Draw the small signal model of the amplifier circuit (3 marks)
- Calculate the amplifier input and output impedances (2 marks)
- Calculate the amplifier mid-band gain (4 marks)
- Calculate the lower cut-off frequency of the amplifier (5 marks)

4. A BJT-based amplifier circuit is illustrated in figure 4.

- Design resistor component values to provide midband gain  $A_v = 520$  assuming  $I_C = 3\text{mA}$ . Assume also that  $R_i = 2.4\text{k}\Omega$ . (10 marks)


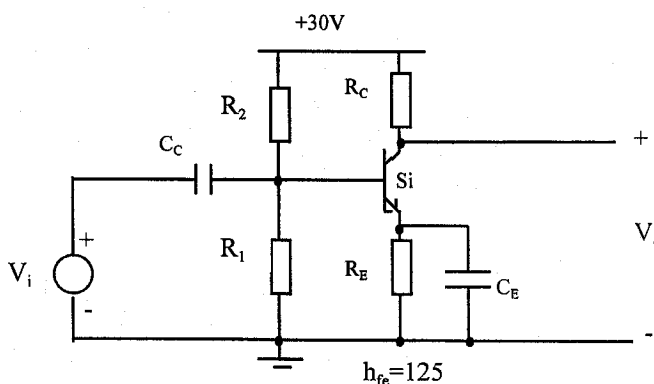


Figure 4 Common Emitter Amplifier

- Design, using a zener diode a 10 volt regulated power supply to handle load currents of 0 - 500 mA. The input voltage available is an unregulated supply which can vary over the range of 30 - 45 volts. You should allow at least 25 mA zener current under worst-case conditions to ensure that the zener is operating in its active region. (6 marks)
- Calculate the maximum power dissipated in the zener and select a suitable power rating for this device. What are the main disadvantages of this simple zener regulator? (4 marks)

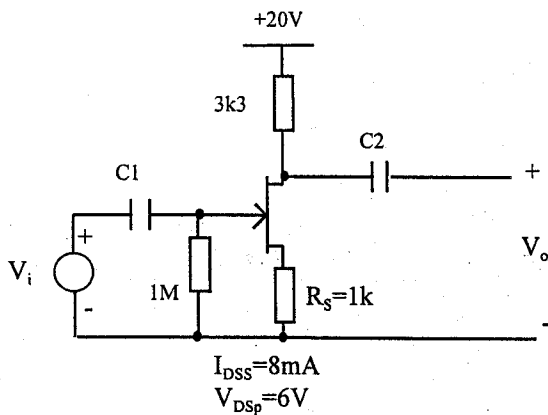5. a) Illustrate n-channel JFET device operation modes using cross sectional diagrams and  $I_{ds}-V_{ds}$  characteristics (4 marks)
- b) Explain the role of the resistor in the source path of the FET amplifier circuit (figure 5) (3 marks)
- c) Calculate the d.c. operating point of the FET amplifier (6 marks)
- d) Sketch the small signal model for the amplifier circuit (3 marks)
- e) Calculate the amplifier mid-band gain (4 marks)



$$I_{DSP} = I_{DSS} \left( 1 - \frac{V_{GS}}{V_{GS(cut-off)}} \right)^2$$

Figure 5 JFET Amplifier

6. Figure 6 shows a temperature sensing circuit using a silicon sensor  $R_t$ . The sensor resistor has the following characteristics :

$$R_t = 825\Omega \text{ at } 0^\circ\text{C}$$

$$R_t = 1.8k\Omega \text{ at } 100^\circ\text{C}$$

- a) Calculate the value of  $R_x$  which gives  $V_o = 0V$  at  $0^\circ\text{C}$  (8 marks)
- b) Calculate the value of  $V_o$  at  $100^\circ\text{C}$  (7 marks)

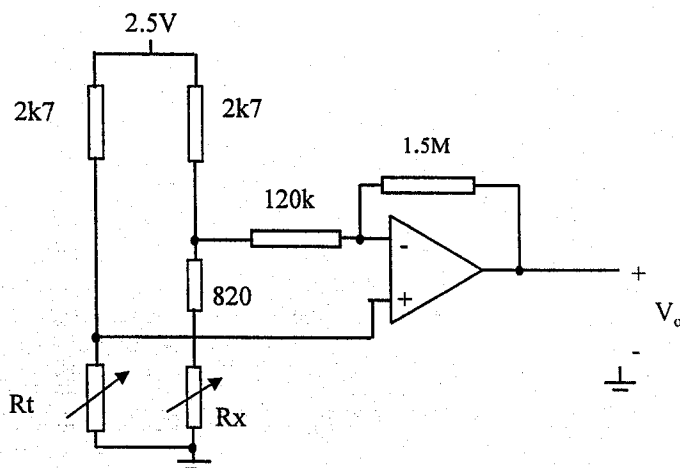


Figure 6 Temperature sensor

- c) Sketch a 'super diode' precision rectifier circuit and explain its operation and application. (5 marks)

- 7.
- a) Draw the circuit for a Schmitt trigger. Explain its operation and derive the input switching voltage values. (5 marks)
  - b) Draw the circuit diagram of a differential amplifier and explain its principle of operation (include a current source in the emitters' circuit). (4 marks)
  - c) Draw the small signal equivalent circuit model for a single ended differential amplifier and derive the expression for the small signal differential gain (6 marks)
  - d) Explain the following as they apply to operational amplifiers and illustrate (with waveform diagrams), the effect of each on the op-amp output signal. (5 marks)
    - (i) Input Offset Voltage
    - (ii) Slew rate
    - (iii) CMRR