

OLLSCOIL NA hÉIREANN, GAILLIMH  
NATIONAL UNIVERSITY OF IRELAND, GALWAY

AUTUMN EXAMINATIONS, 1999

FIRST ELECTRONIC ENGINEERING  
FIRST ELECTRONIC AND COMPUTER ENGINEERING  
FIRST INDUSTRIAL ENGINEERING  
FIRST UNDENOMINATED ENGINEERING

ANALOGUE ELECTRONICS

Professor L.E. Davis  
Professor D. J. Wilcox  
Mr. F. C. O'Malley

Duration of examination: *Two* hours

Instructions: Answer *four* questions

1. Using Kirchoff's Laws determine the current flowing in each branch of the circuit of figure 1.1 below. Indicate the voltage that exists across each resistor and specify the total power delivered by the battery to the circuit.

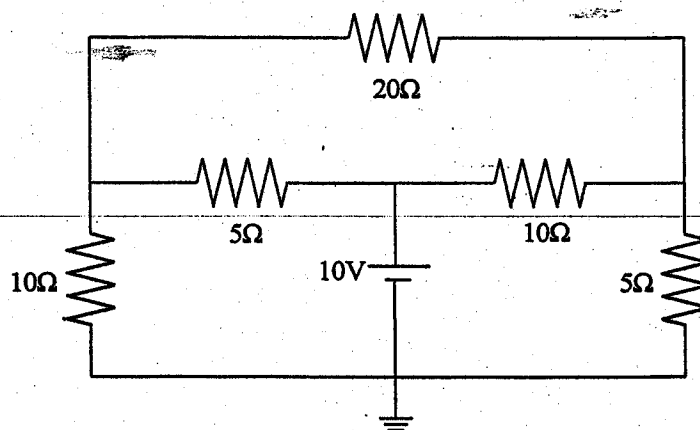


Figure 1.1

2. (a) The load resistor, of the circuit of figure 2.1 is to be attached between terminals A and B as indicated. You are required to calculate the Thévenin equivalent of the circuit without the load connected.
- Determine the open circuit voltage  $V_{AB}$ .
  - Determine the short circuit current  $I_{AB}$ .
  - Draw the Thévenin equivalent circuit.

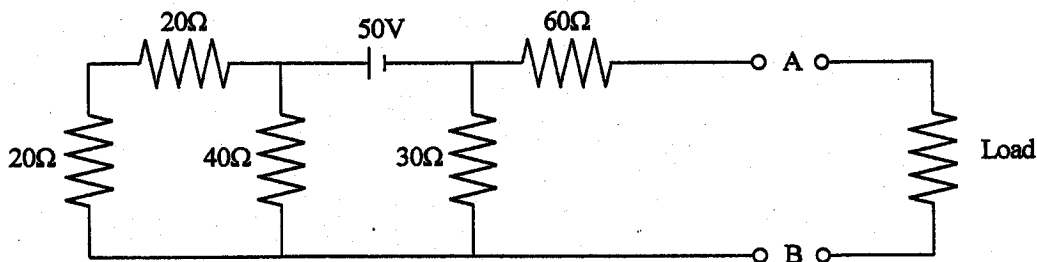


Figure 2.1

- (b) By attaching the load resistor,  $R_L = 60\Omega$ , to the equivalent circuit determine the voltage across this load and the current through it. What value of load resistance would draw maximum power from the supply.

3. (a) Explain what is meant by the principle of superposition as applied to electrical circuits.
- (b) Using the principle of superposition determine the current  $I$ , flowing in the  $2k\Omega$  resistor in the circuit of figure 3.1.

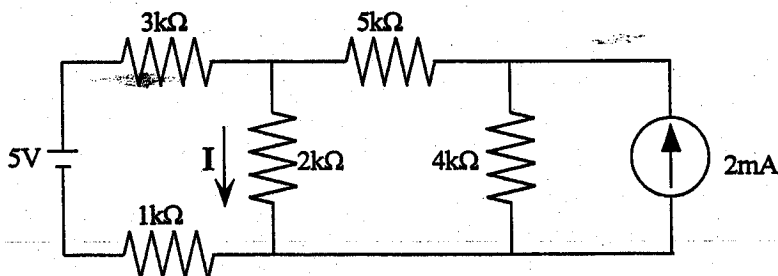


Figure 3.1

4. Determine the magnitude of the currents  $I_R$ ,  $I_L$  and  $I_C$  in the circuit as of figure 4.1. Plot each of these on a phasor diagram. Proceed to determine the magnitude of the supply current  $I_s$  and plot it also on the phasor diagram. Specify exactly the phase relationship between the supply current and supply voltage. Finally, plot two cycles of both  $i_s(t)$  and  $v_s(t)$ .

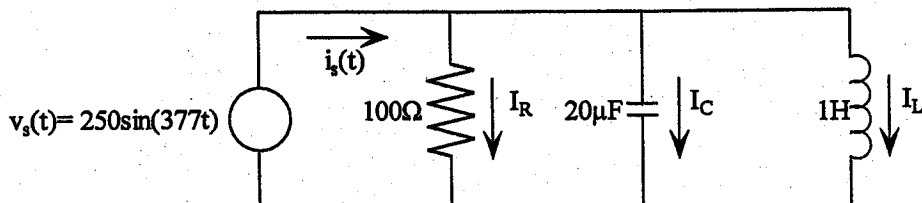


Figure 4.1

5. For the circuit of figure 5.1 use a phasor diagram to determine the magnitude and phase angle of the following variables:  $V_L$ ,  $V_R$ ,  $V_C$ ,  $I_S$  and  $V_S$ . Your phasor diagram should include a representation of each of above. Also, plot one cycle of the supply voltage and current.

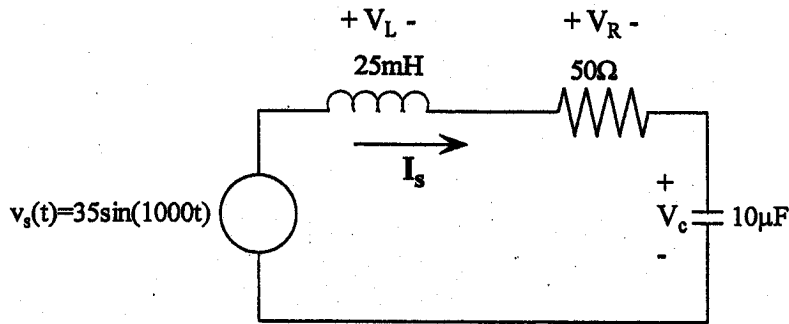


Figure 5.1

6. (a) Derive an expression for the rms value of a full-wave rectified sinusoidal signal of period  $T$  and peak voltage  $V_p$ .
- (b) The circuit of figure 6.1 shows a half wave rectifier. Plot two cycles of the output voltage  $v_o(t)$  and output current  $i_o(t)$ . What is the power dissipated in the  $1k\Omega$  load resistor.

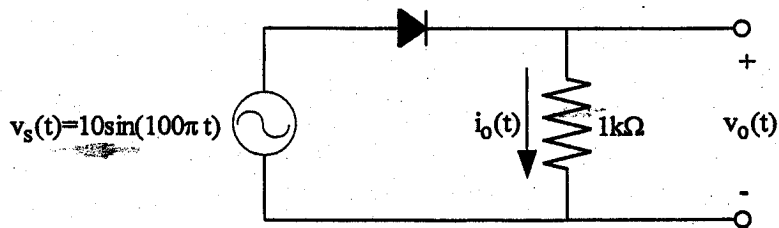


Figure 6.1

- (c) A smoothing capacitor is to be added to the circuit. Calculate the value of capacitance necessary in order to keep the ripple of the output voltage below 10%. Plot two cycles of the smoothed output voltage waveform.